
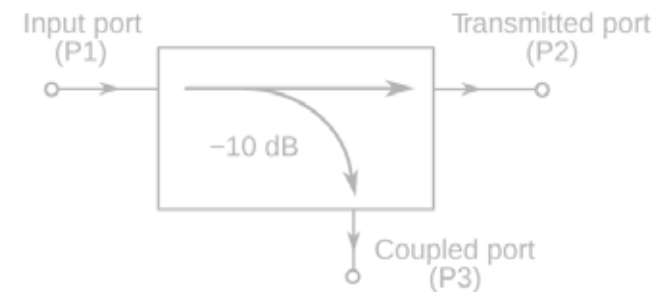


Microwave Engineering

MCC121, 7.5hec, 2014

Lecture 8 Passive devices

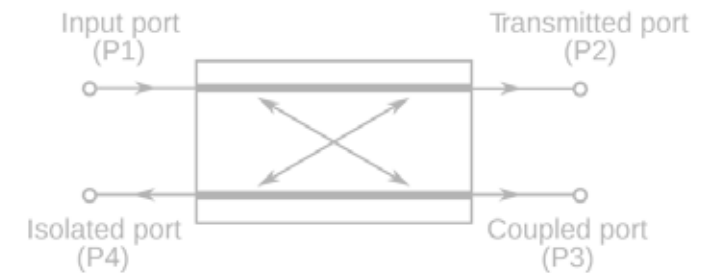

*State-of-the-art
Challenging
Stimulating
Rewarding*

Outline

- Summary of lecture 7 (Ch5)
- Passive microwave devices
 - attenuators, loads
 - phase shifters
 - power dividers (7.1-7.4)


Objectives

On completion of this course unit you should be able to:


- Analyse wave propagating properties of guided wave structures (TE, TM, TEM waves, microstrip, stripline, rectangular and circular waveguides, coupled lines)
- Apply N-port representations for analysing microwave circuits
- Apply the Smith chart to evaluate microwave networks
- Design and evaluate impedance matching networks
- Design, evaluate and characterise directional couplers and power dividers
- Design and analyse attenuators, phase shifters and resonators
- Explain basic properties of ferrite devices (circulators, isolators)

Transformers

Tapered transformer

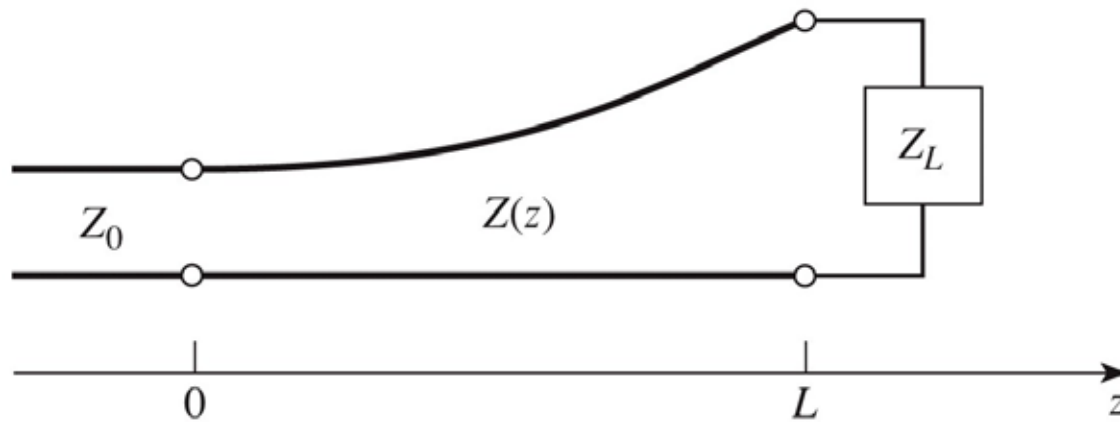

(a)

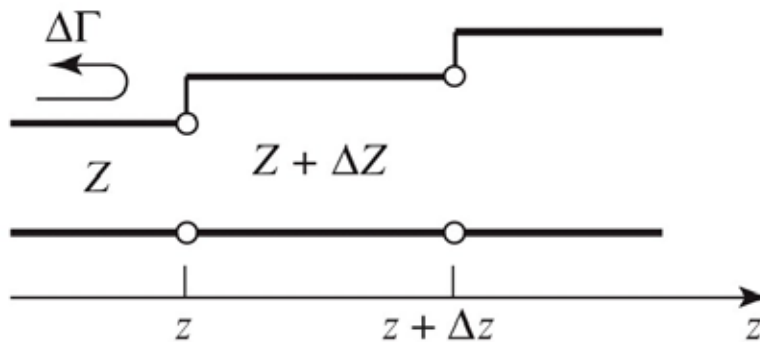


(b)

$$d\Gamma_{in} = e^{-2j\beta z} \frac{1}{2} \frac{d}{dz} (\ln Z) dz$$


$$\Gamma_{in} = \int_0^L d\Gamma_{in} = \frac{1}{2} \int_0^L e^{-2j\beta z} \frac{d}{dz} (\ln Z) dz \quad (1)$$

Figure 5.18
© John Wiley & Sons, Inc. All rights reserved.

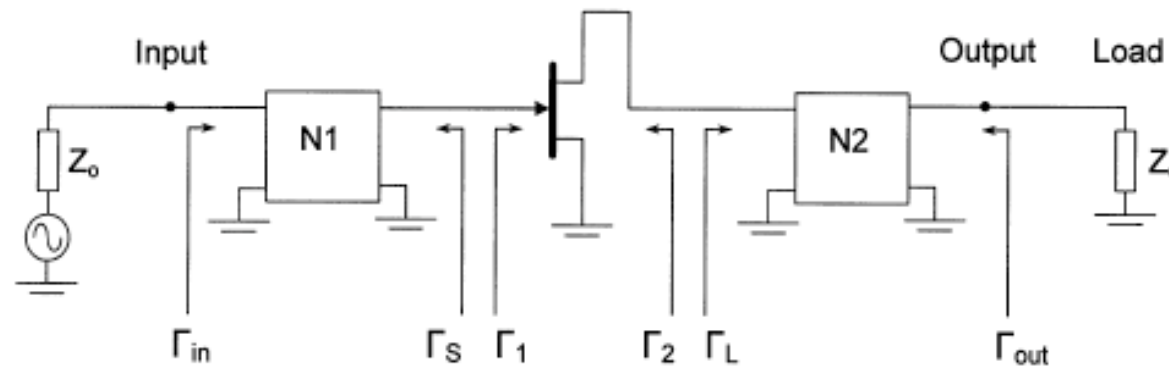


Design of complex impedance terminations

Ex) design of amplifier

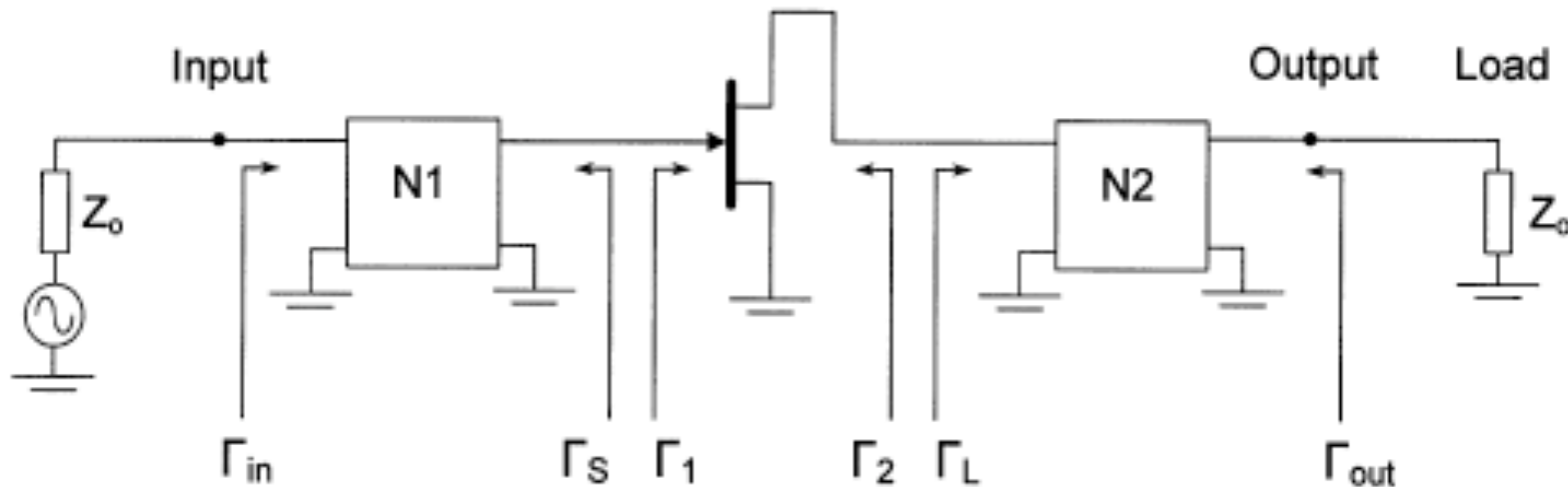

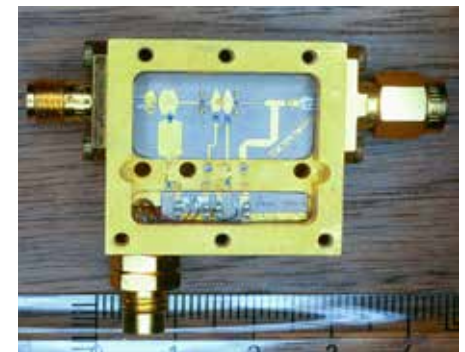
- Find Gamma-S &-L for a certain noise, gain, stability requirements... (more about this in active microwave circuits)
- Synthesise matching networks N1 and N2 to provide these complex impedances (This course MCC121)



Courtesy of Niklas Wadefalk
MC2, Chalmers and
Low Noise Factory

Passive microwave devices



Terminations

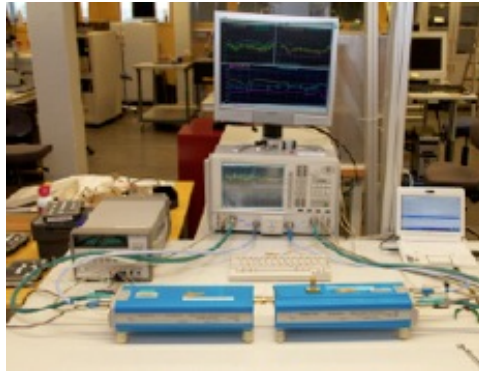

Common μ -wave lab utensils


- Matched load $\Gamma = 0$
- Variable short circuit $\Gamma = 1 \cdot e^{j\phi}$

Ex) Matched loads

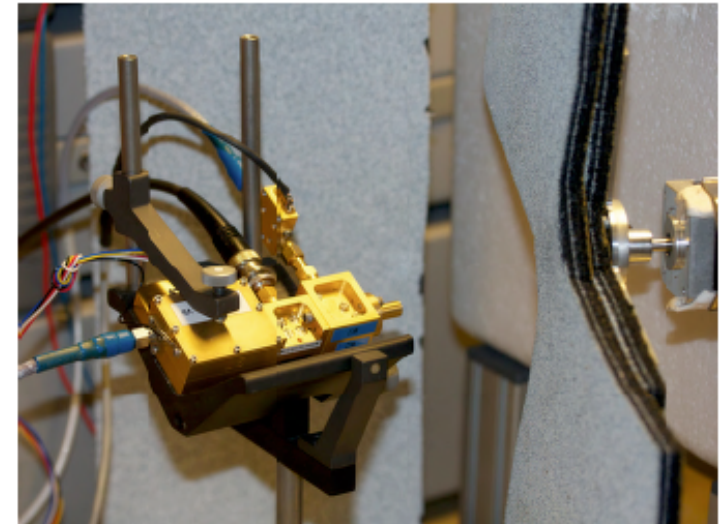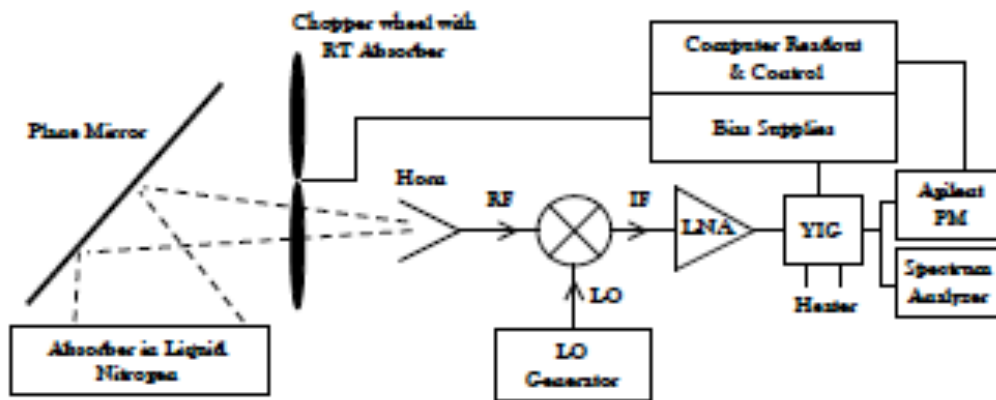


- Noise figure measurement (Y-factor measurement using two loads at two different temperatures)
- Termination to absorb all power (terminating the line in its characteristic impedance)

matched load

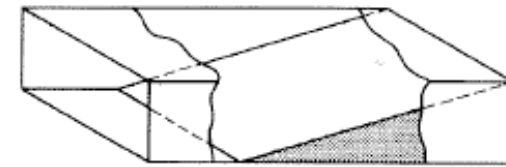


(a)

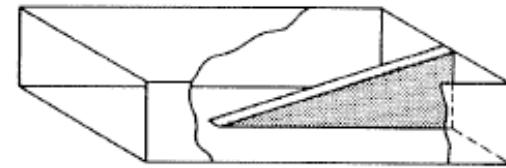

(b)


- "lossy" transmission line
- Reflections are avoided by tapering the lossy material into a wedge

Movable shorts

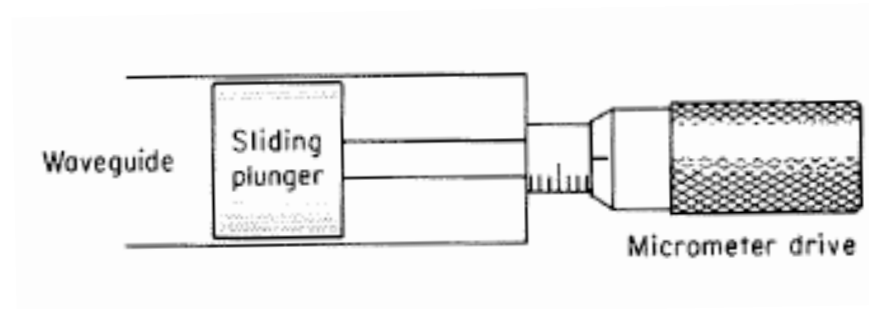

- Impedance tuning element (reactance)

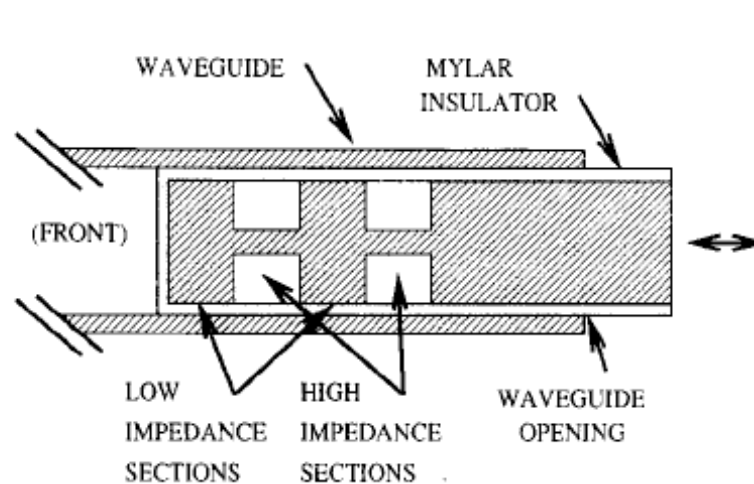The art of making a movable waveguide short



IEEE TRANSACTIONS ON MICROWAVE THEORY AND TECHNIQUES, VOL. 43, NO. 5, MAY 1995

Analysis and Design of a Novel Noncontacting Waveguide Backshort

Thomas M. Weller, *Student Member, IEEE*, Linda P. B. Katchi, *Senior Member, IEEE*, and William R. McGrath, *Member, IEEE*

$$Z_{RF} = \left(\frac{Z_{low}}{Z_{high}} \right)^n Z_{low}$$

- Contacting versus noncontacting shorts
 - Contacting wear out + hard to achieve perfect contact
- Solution: High and low impedance quarter wave sections (guided wave). Or apply filter theory...

Dual-Harmonic Noncontacting Millimeter Waveguide Backshorts: Theory, Design, and Test

MICHAEL K. BREWER AND ANTTI V. RÄISÄNEN


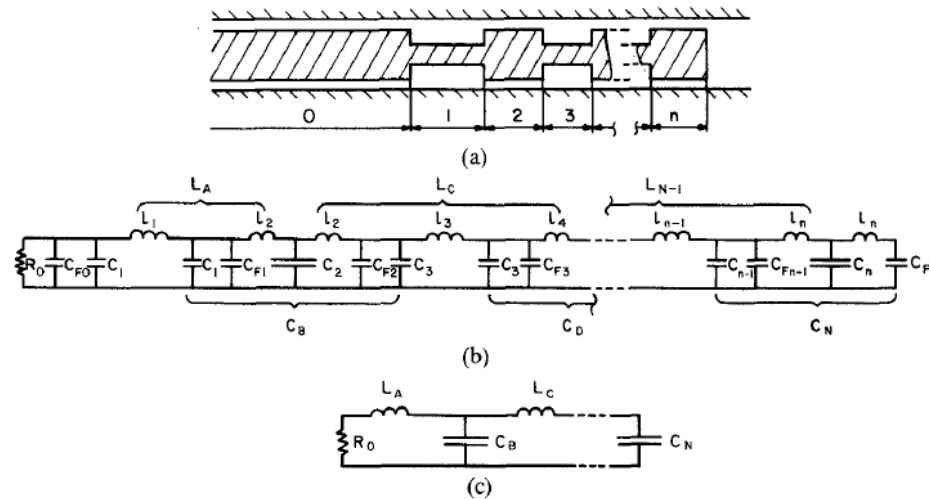


Fig. 1. (a) Alternating high-low impedance noncontacting backshort. (b) Quasi-lumped circuit. (c) Lumped circuit.


filter theory -> synthesise a band stop filter (high VSWR)

Rotary attenuator

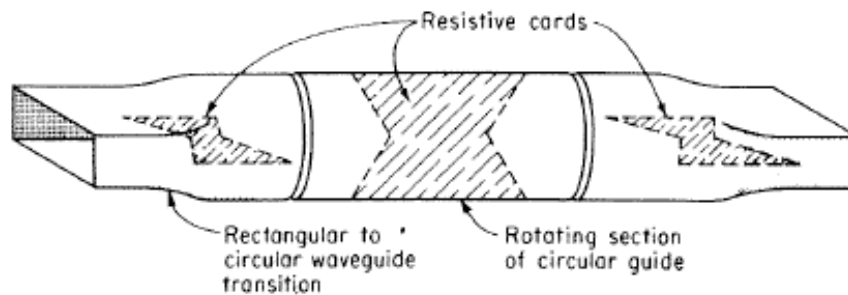


- Precision attenuator with low VSWR. The attenuation is insensitive to frequency; variations of phase with attenuation are negligible.
- Lab equipment rather than employed in systems.



Decomposition of TE_{11} mode

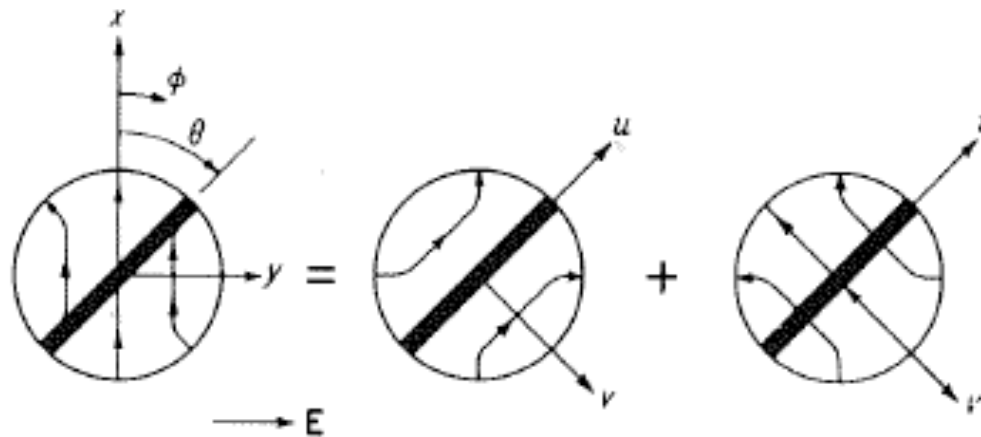

Sum of two orthogonally polarized modes

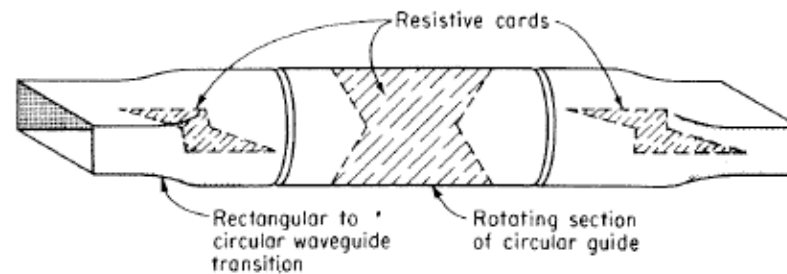


Resistive T or Pi -attenuator

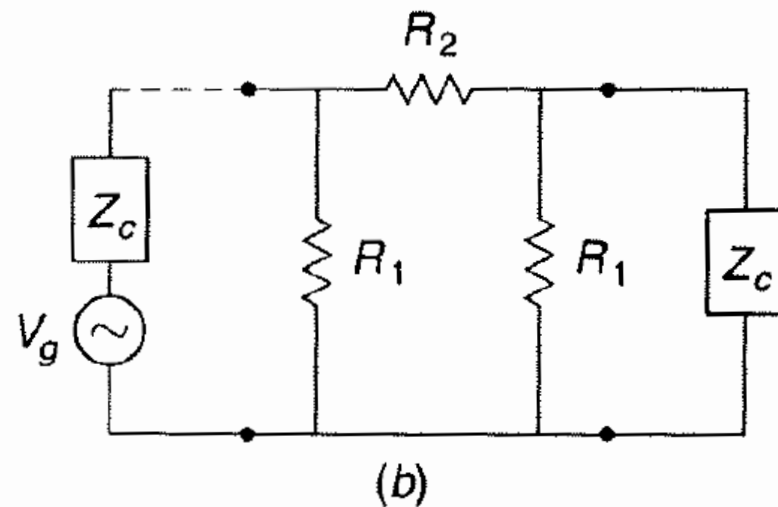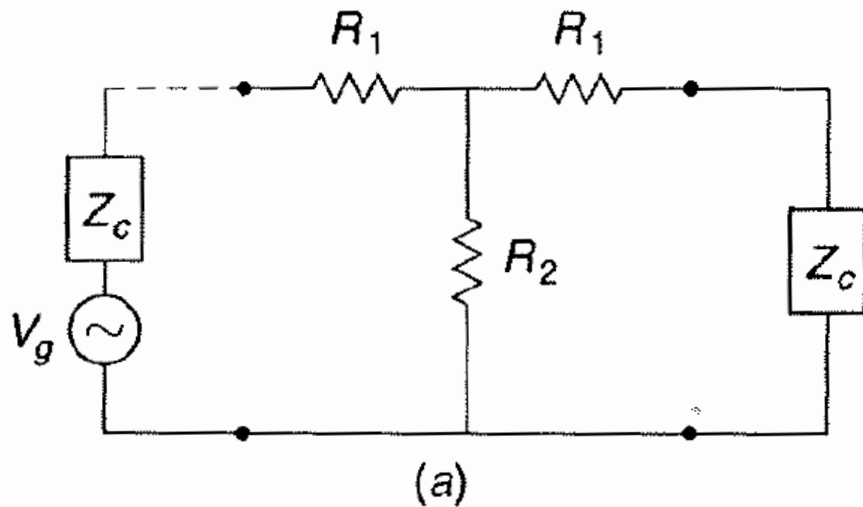

$$[S] = \begin{bmatrix} 0 & k \\ k & 0 \end{bmatrix}$$



- *On white board: Derive a set of design equations for a resistive attenuator (T).*

3-dB attenuator

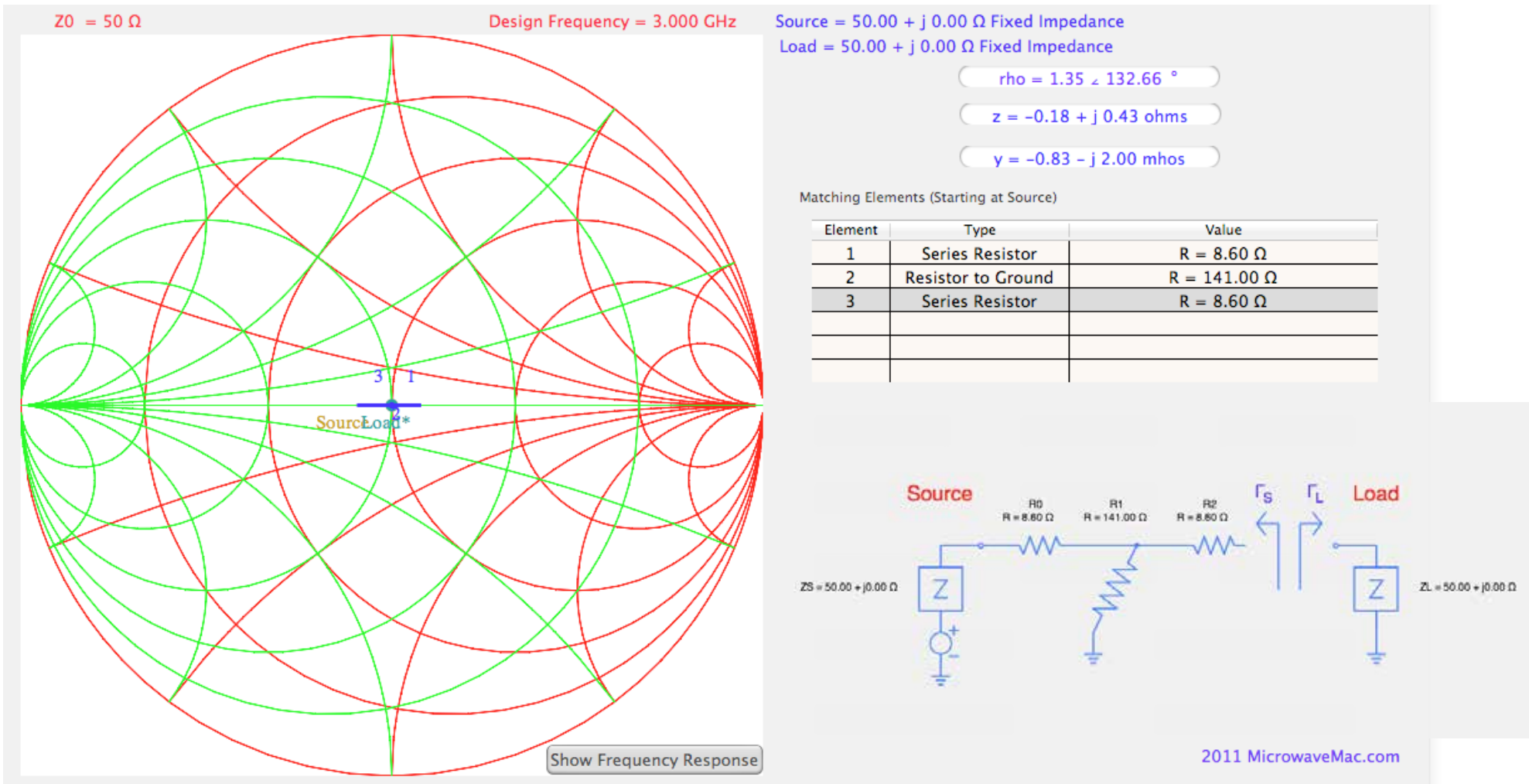

Explain the different "moves" in the Smith Chart. Can we replace the shunt resistor to avoid via-hole to ground.

Resistive T or Pi -attenuator

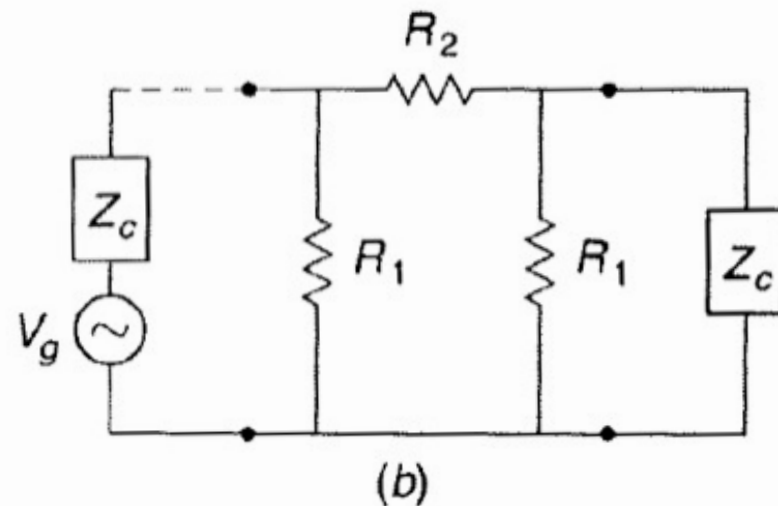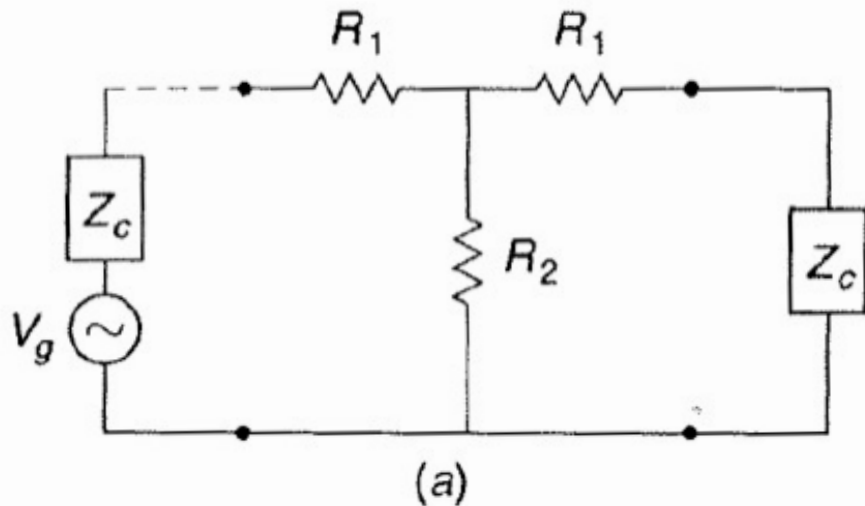


$$[S] = \begin{bmatrix} 0 & k \\ k & 0 \end{bmatrix}$$

Phase shifter

- Phase shifters are components used to control the phase of a signal with lowest possible influence on the amplitude.
- There are many different types of phase shifters depending on the used technology.


Switched line phase shifter

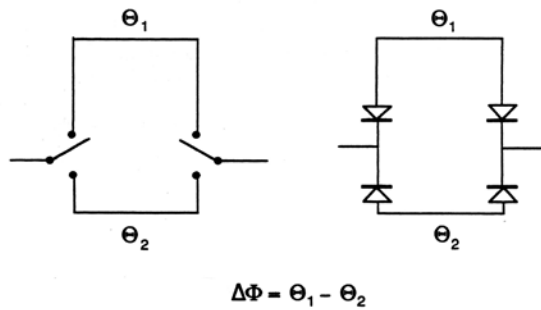

$$\Delta\phi(f) = \theta_1(f) - \theta_2(f) = \theta_1|_{f=f_0} \frac{f}{f_0} - \theta_2|_{f=f_0} \frac{f}{f_0} =$$

$$= \beta \left(l_1 \frac{f}{f_0} - l_2 \frac{f}{f_0} \right)$$

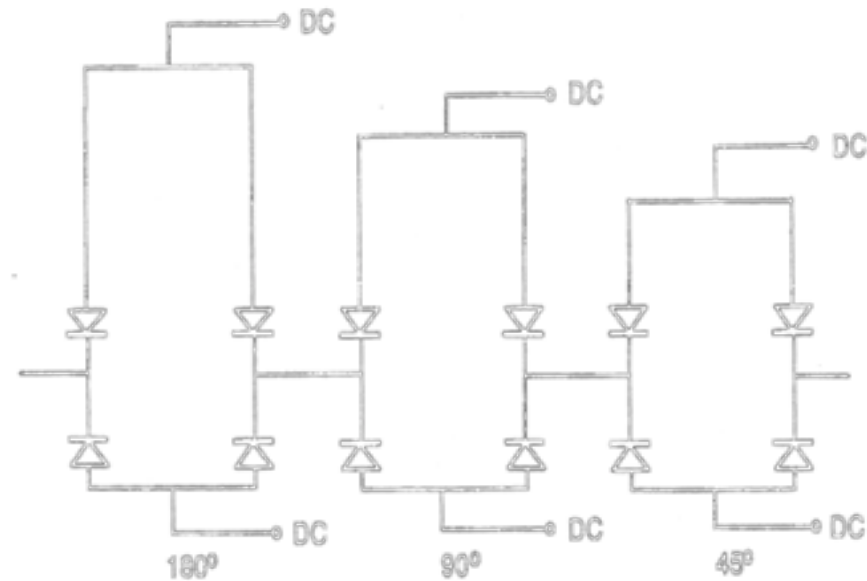- The losses are constant at all states
- The circuit is very simple
- The circuit is small



- Each bit needs at least 4 diodes, high power consumption
- Complicated DC supply

© J. Piotr Starski

Differential phase shifters

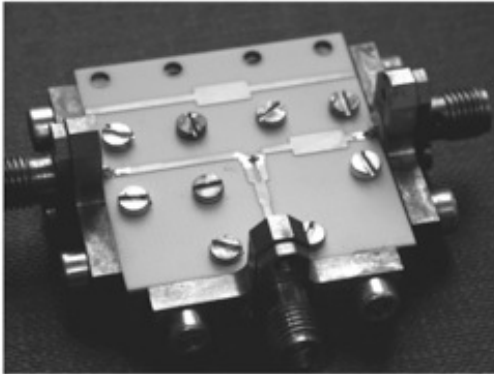


Fig. 10 Photograph of the coaxial test fixture with an assembled phase shifter circuit. A 100 Ω 0402-thin-film resistor chip was used for the Wilkinson divider odd mode termination

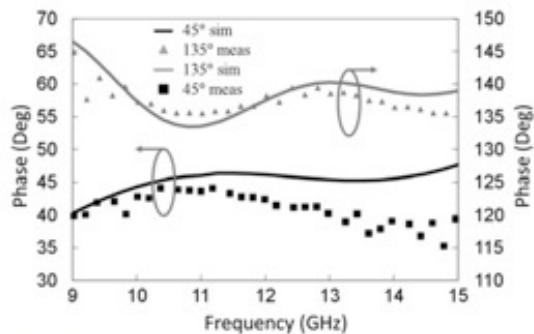


Fig. 11 Simulated (line) and measured (dot) differential phase of the 45° (black) and 135° (grey) differential phase shifter circuits

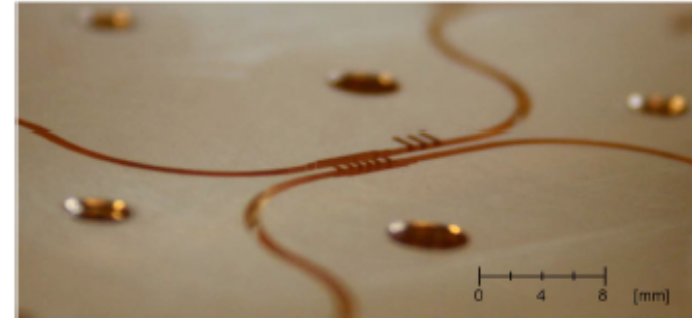


Fig. 2. Photograph of the WR-05 waveguide phase shifter hybrid manufactured in an E-plane split block.


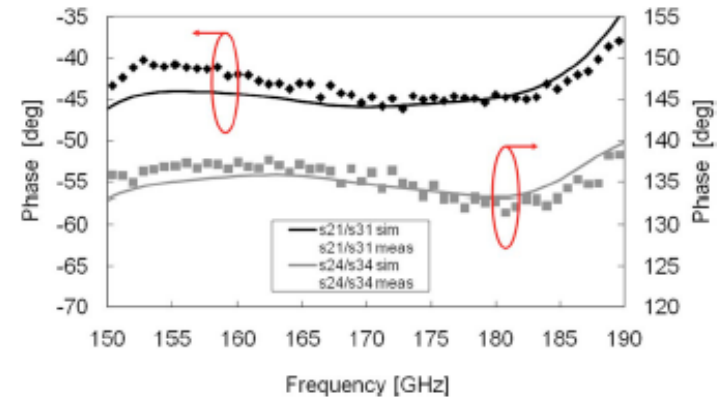


Fig. 3. Simulated (solid) and measured (dot) phase imbalance.

from P. Sobis, J. Stake, and A. Emrich, "High/low-impedance transmission-line and coupled-line filter networks for differential phase shifters," *IET Microwaves, Antennas & Propagation*, vol. 5, no. 4, pp. 386–392, 2011.


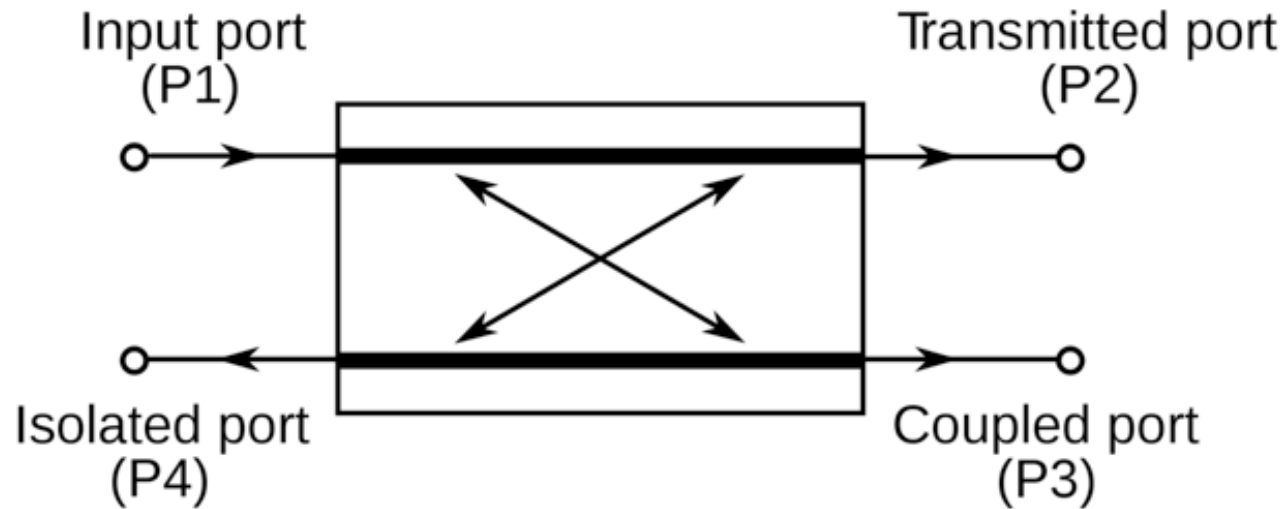
from P. Sobis, J. Stake, and A. Emrich, "A 170 GHz 45° Hybrid for Submillimeter Wave Sideband Separating Subharmonic Mixers," *IEEE Microwave and Wireless Components Letters*, vol. 18, no. 10, pp. 680–682, Oct. 2008.



Directional couplers

Properties

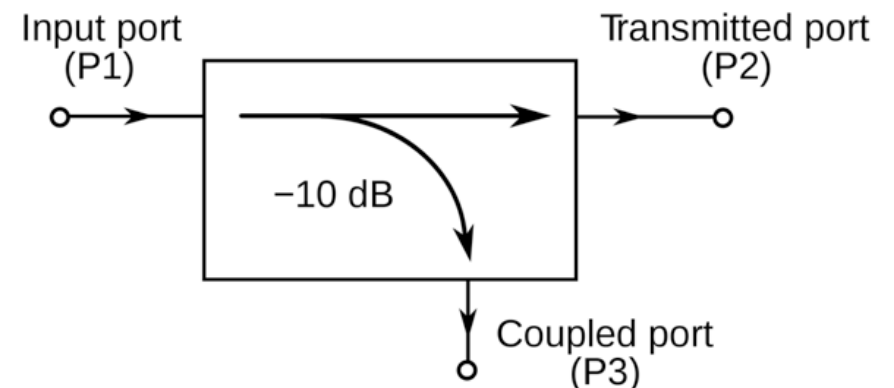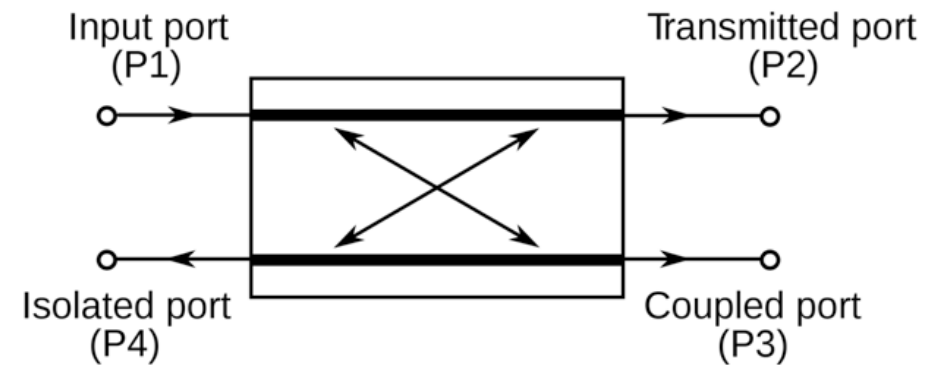- All ports matched
- Ex) Incident power at port 1 couples to port 2 and 3, but not into port 4. Hence, ports 1 & 4 are uncoupled



Applications

- Power monitoring
- Impedance measurement (reflectivity)
- Power dividers (distributing networks)

S-parameter test set-up


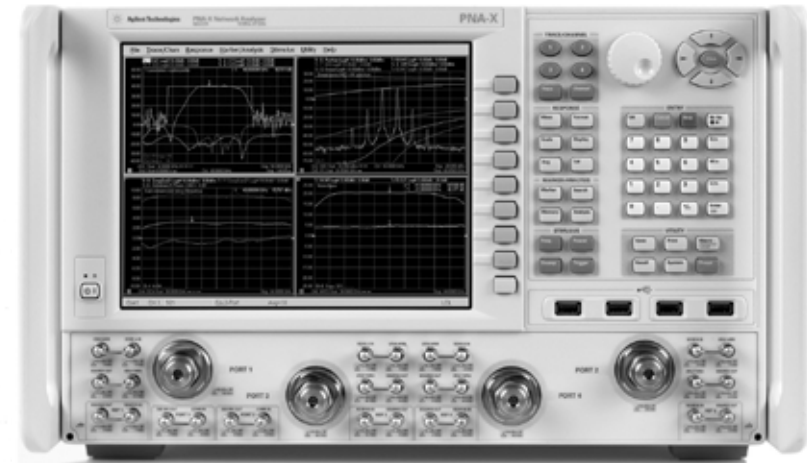
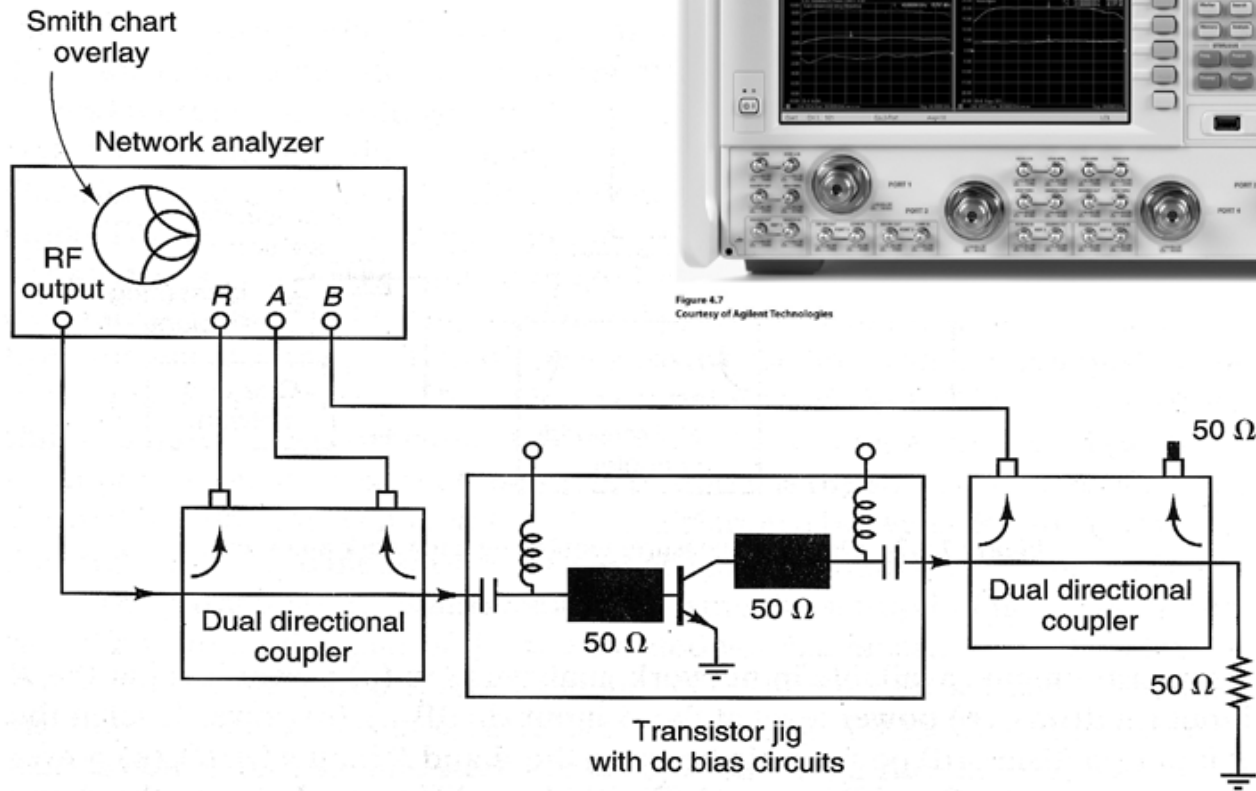



Figure 4.7
Courtesy of Agilent Technologies

Power combining networks

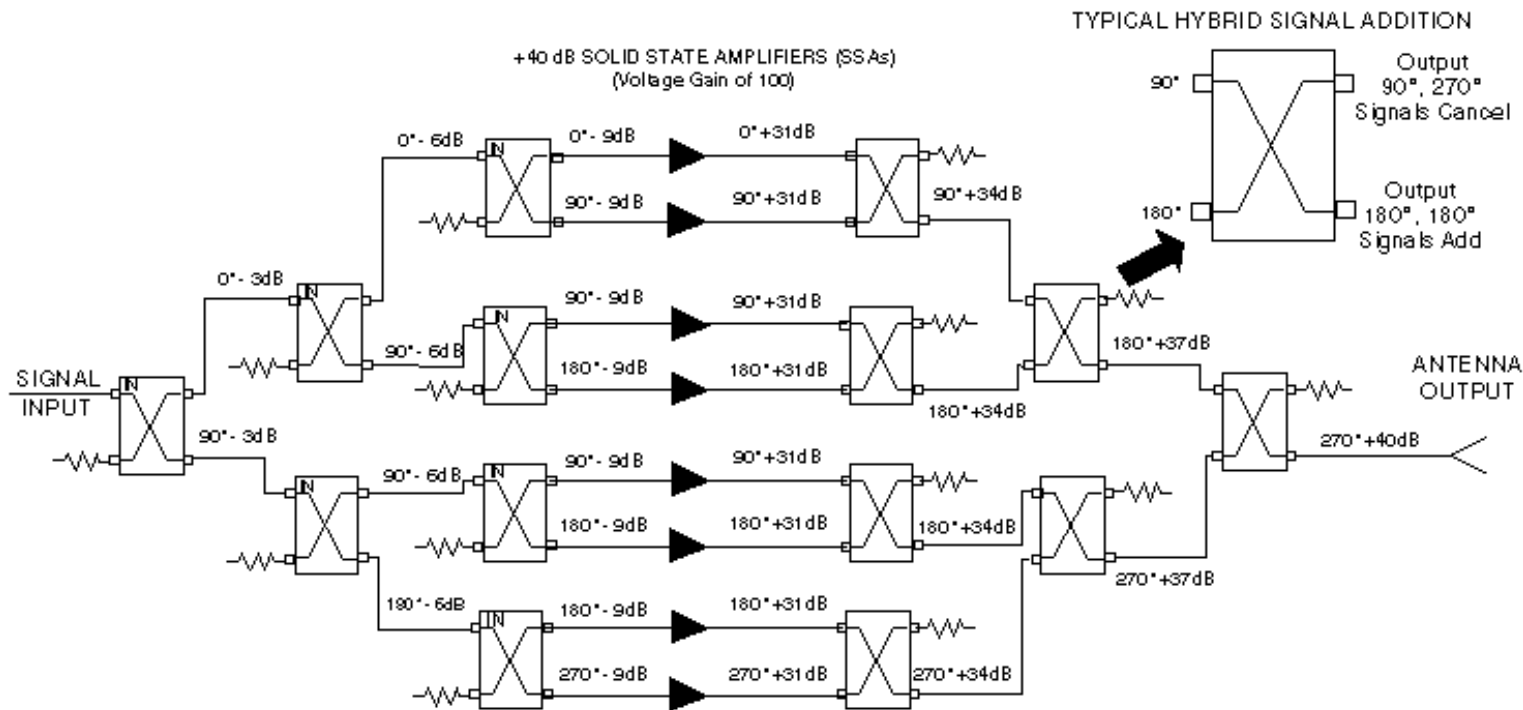

NOTE: All isolated ports of the hybrids have matched terminations. They have signals which are out of phase and cancel

Figure 6. Combiner Network

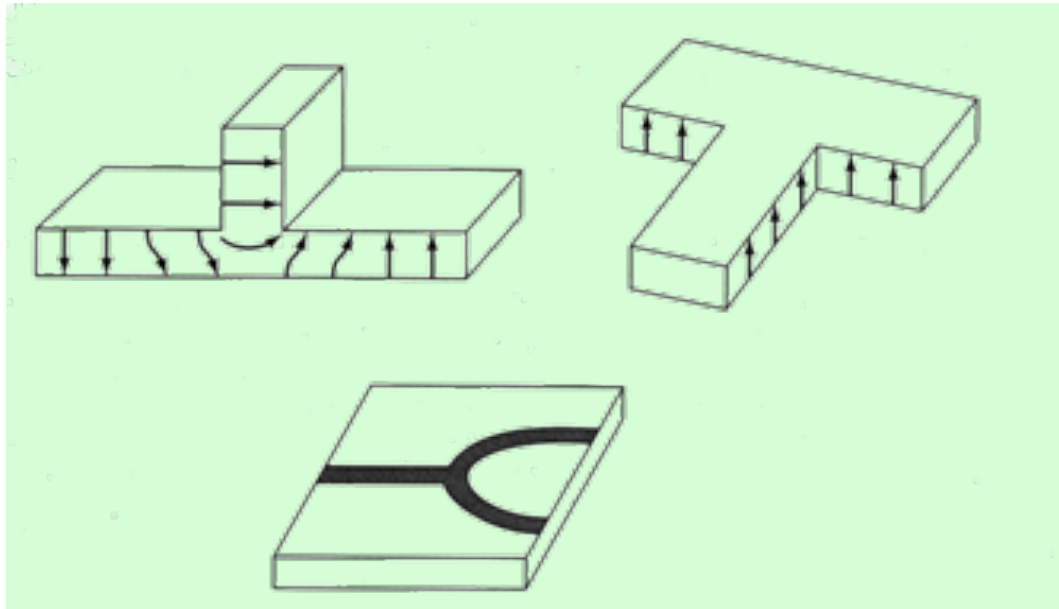

Power dividers

Power dividers or combiners

- Power divider is used to divide input power among several outputs

- We want:

- reciprocal

- lossless



- matched

$$[S] = \begin{bmatrix} 0 & s_{12} & s_{13} \\ s_{12} & 0 & s_{23} \\ s_{13} & s_{23} & 0 \end{bmatrix}$$

Impossible!
must relax one of the conditions

- *On white board: Derive properties for a passive reciprocal 3-port*


Lossless divider

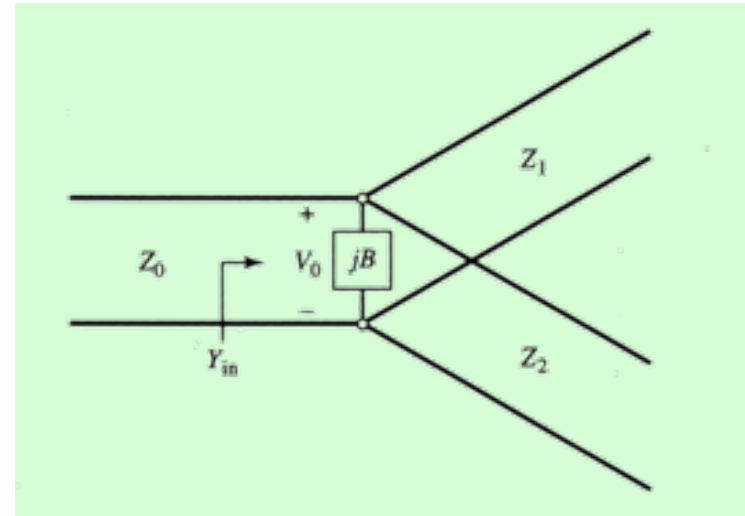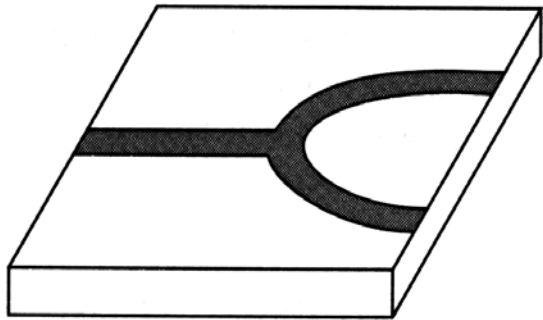

Can not be matched at all ports, and no isolation!

- *On white board: Show that a 2-way lossless divider (three-port junction) can not be simultaneously matched.*


Resistive divider

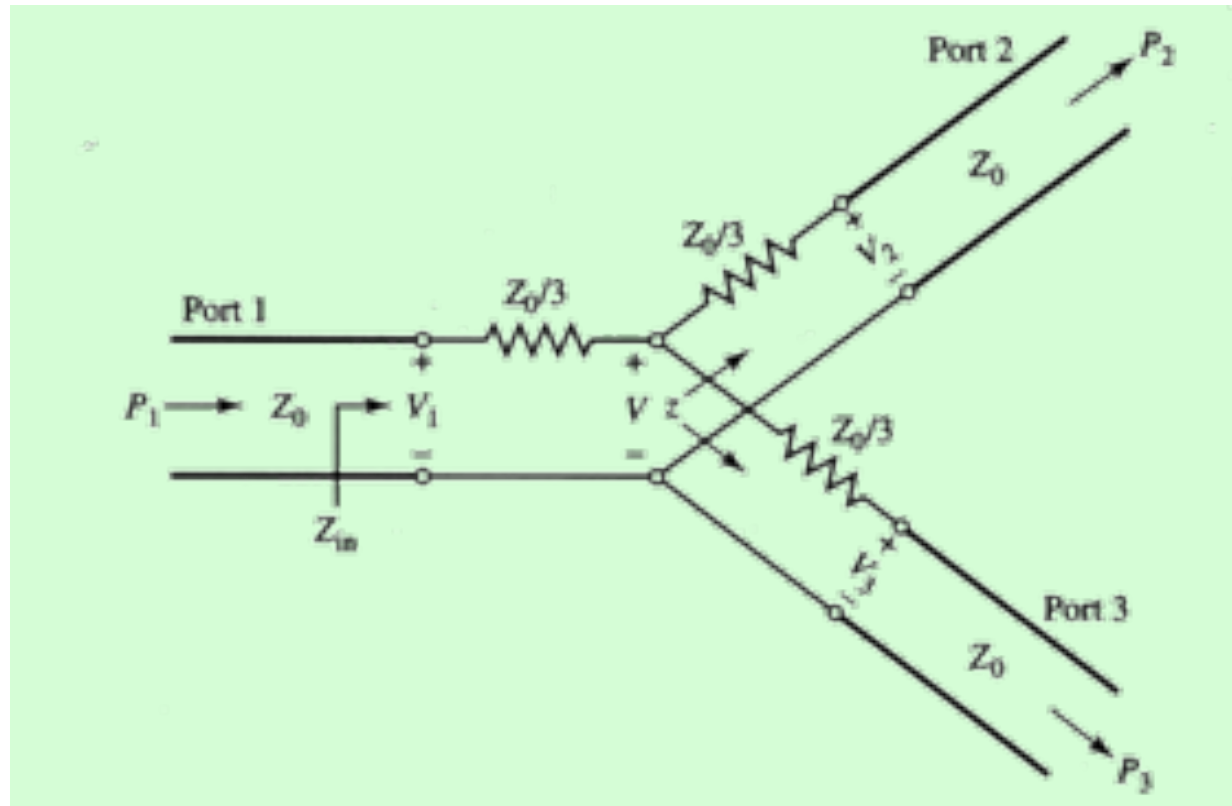

Lossy and reciprocal, thus can be matched at all ports

No isolation!

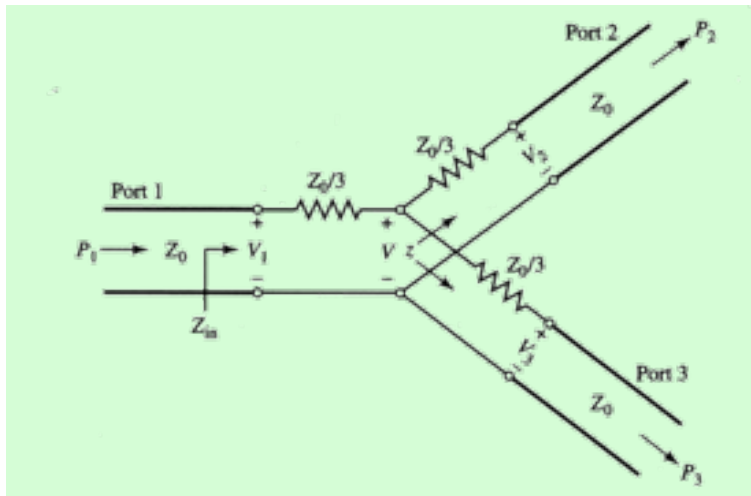- *On white board: Derive properties for a 3-port resistive divider.*



$$[s] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

No isolation

The matrix is not unitary!!!!


$$[s]^* \neq \left\{ [s]^T \right\}^{-1}$$

$$P_{in} = \frac{1}{2} \frac{V_1^2}{Z_0}; P_2 = P_3 = \frac{1}{2} \frac{\left(\frac{1}{2} V_1\right)^2}{Z_0} = \frac{1}{8} \frac{V_1^2}{Z_0} = \frac{1}{4} P_{in}$$

Half of the incident power is lost in the power divider


The Wilkinson power divider

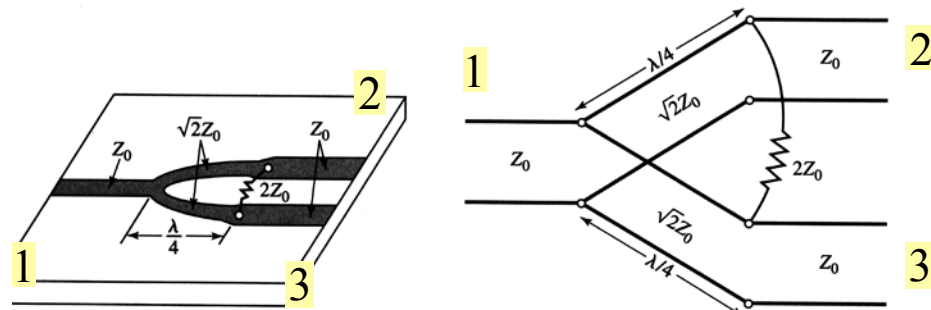- The Wilkinson power divider is lossless, when the output ports are matched, and has isolation between the output ports.



Even and odd mode method


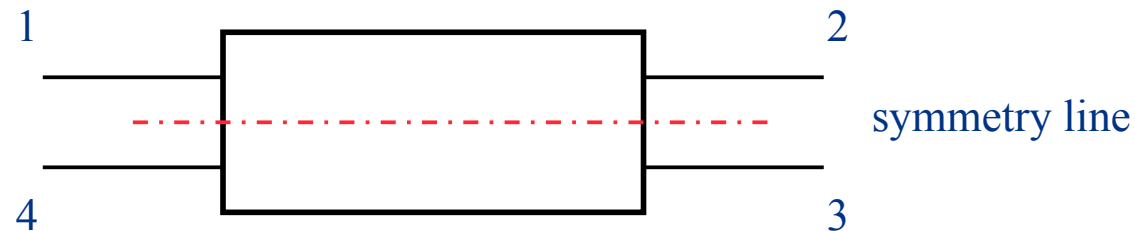
Consider a **linear, reciprocal** 4-port with a **symmetry** line as marked




We will analyze this circuit by using the *even* and *odd mode* method. The method is based on two excitations: even and odd, applied to the ports on opposite sides of the symmetry line (in our case port 1 and 4). The even excitation corresponds to two voltages equal in amplitude and phase, e.g. +1 V. The odd excitation corresponds to two voltages equal in amplitude but with 180° phase difference (+1 V, and -1 V).

By applying the **even excitation** to the ports 1(+1 V), and 4(+1 V) the symmetry line will act as an **open circuit** or as we say **magnetic wall**.

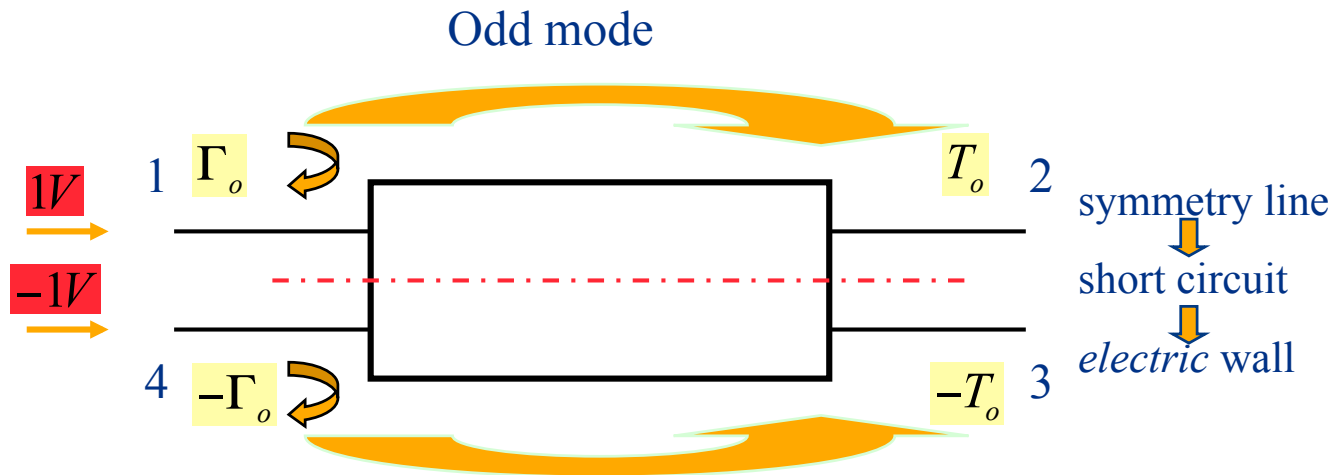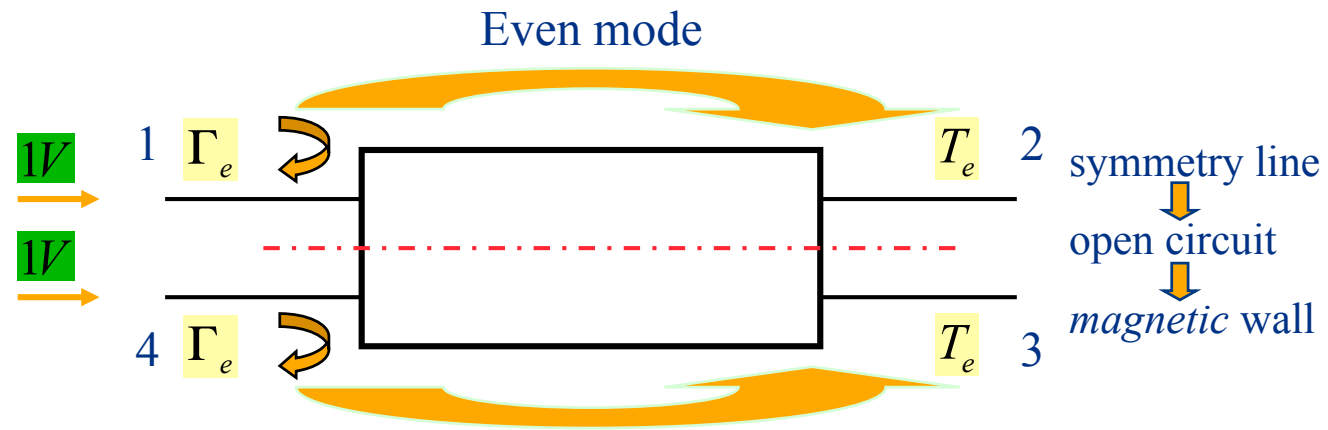By applying the **odd excitation** to the ports 1(+1 V), and 4(-1 V) the symmetry line will act as a **short circuit** or as we say **electric wall**.




We superimpose now both excitations:

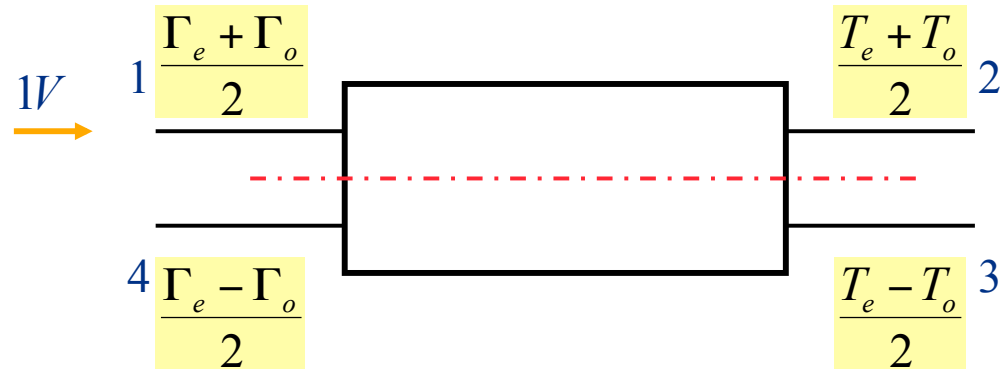

We have only excitation in port 1 and can calculate the reflected and transmitted waves in all ports.

This means that the analysis of a reciprocal, linear 4-port with a symmetry property can be performed by analyzing two 2-ports in two excitation modes and superposition of the results.

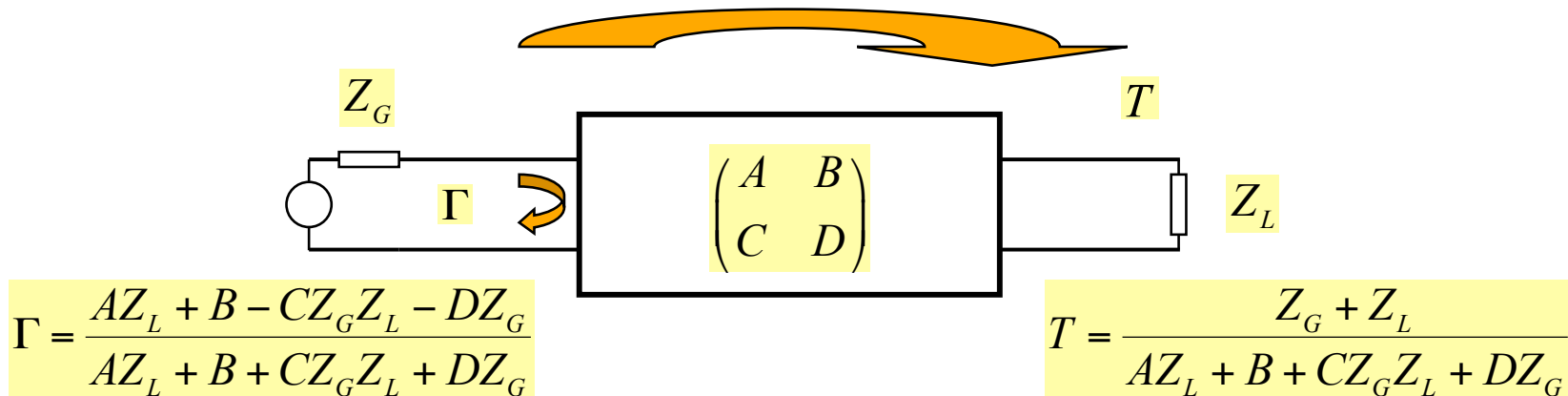
Γ and T for the 2-ports can be easily calculated from the cascade matrix analysis




- *On white board: analyse the Wilkinson divider (3-dB case, three port)*

Wilkinson divider: S matrix

S_{11}

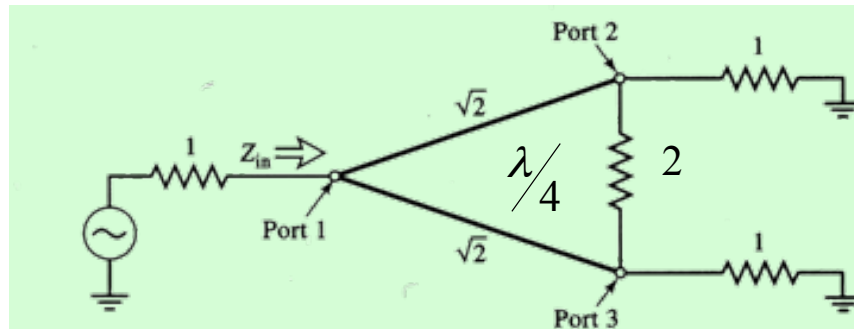

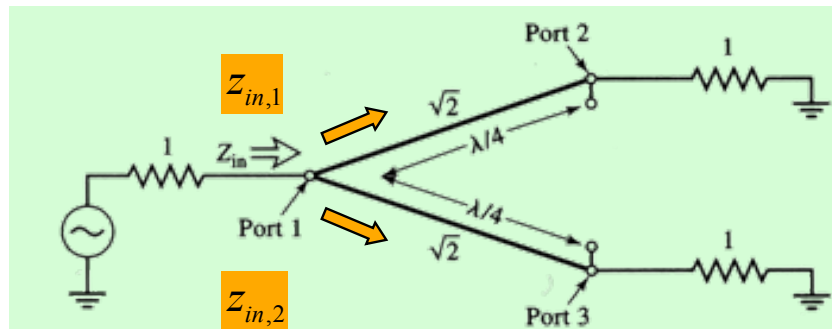The circuit is excited from port 1-
no current through isolating resistor



$$z_{in,1,2} = \frac{(\sqrt{2})^2}{1} = 2; \quad z_{in} = \frac{2 \cdot 2}{2 + 2} = 1$$

$$s_{11} = 0, \text{ since } \Gamma = \frac{z_{in} - 1}{z_{in} + 1}$$

© J. Piotr Starski

Wilkinson divider: S matrix

From previous calculations we have $s_{22} = s_{33}$

$$s_{12} = \frac{V_{1,e} + V_{1,o}}{V_{2,e} + V_{2,o}} = \frac{-j\sqrt{2}\cdot V + 0}{V + V} = -j\frac{1}{\sqrt{2}}$$

$$s_{12} = s_{21}$$

$$s_{13} = s_{31} = s_{12} = -\frac{j}{\sqrt{2}} \quad \text{because the circuit is symmetric}$$

$$s_{23} = s_{32} = 0 \quad \text{depending on the open or short circuit at the symmetry line}$$

$$[s] = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$

ex) 4 way power divider


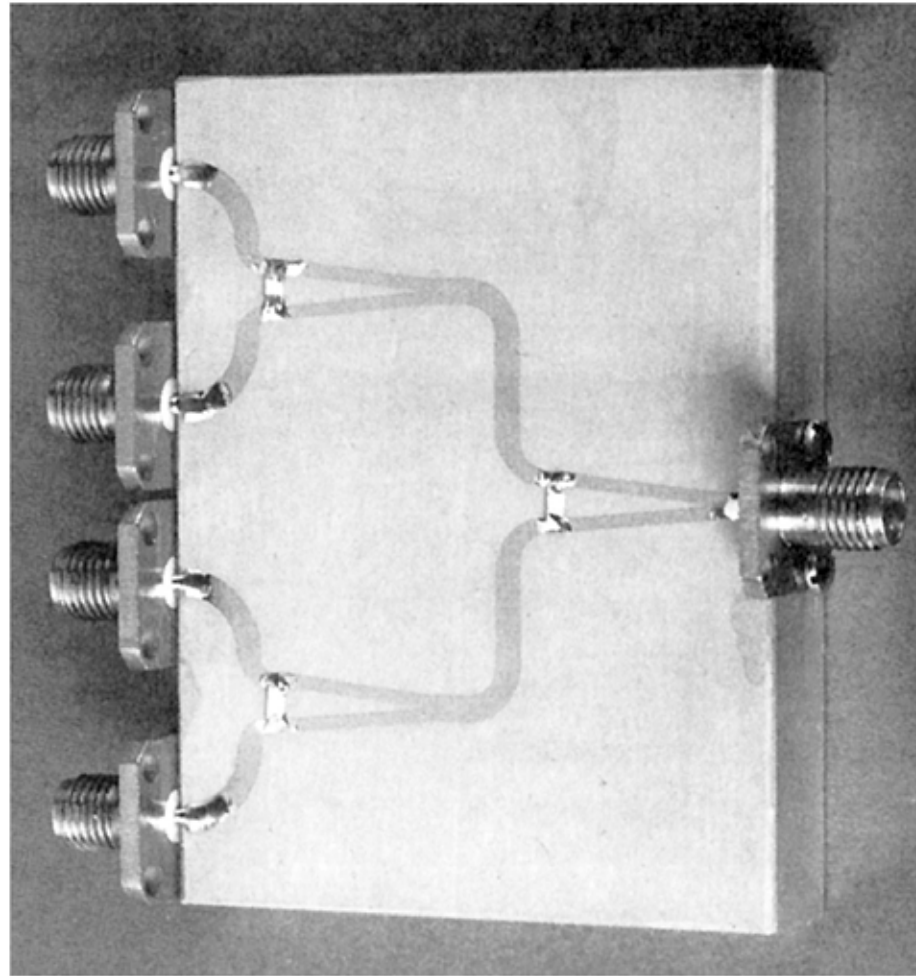



Figure 7.15
Courtesy of M. D. Abouzahra, MIT Lincoln Laboratory, Lexington, Mass.

Wilkinson unequal power divider

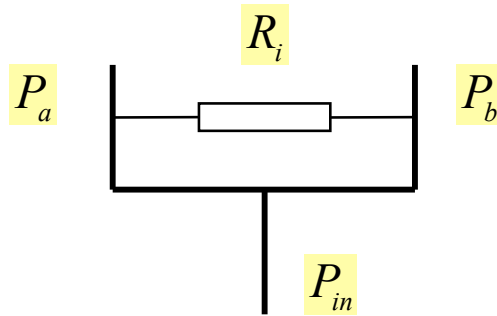

$$\frac{P_b}{P_a} = k^2 \Rightarrow k = \sqrt{\frac{P_b}{P_a}}$$
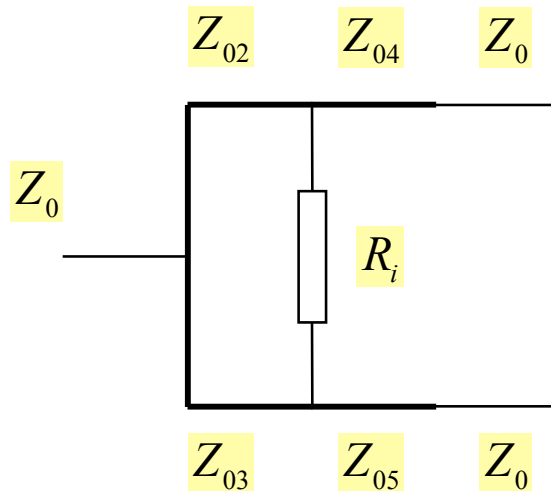
$$\left. \begin{aligned} P_a &= P_{in} \frac{1}{1+k^2} \\ P_b &= P_{in} \frac{k^2}{1+k^2} \end{aligned} \right\} P_a + P_b = P_{in}$$



$$Z_{02} = Z_0 \sqrt{k(1+k^2)}$$


$$Z_{03} = \frac{Z_0}{k} \sqrt{\frac{1+k^2}{k}}$$

$$Z_{04} = Z_0 \sqrt{k}$$

$$Z_{05} = \frac{Z_0}{\sqrt{k}}$$

$$R_i = Z_0 \frac{1+k^2}{k}$$

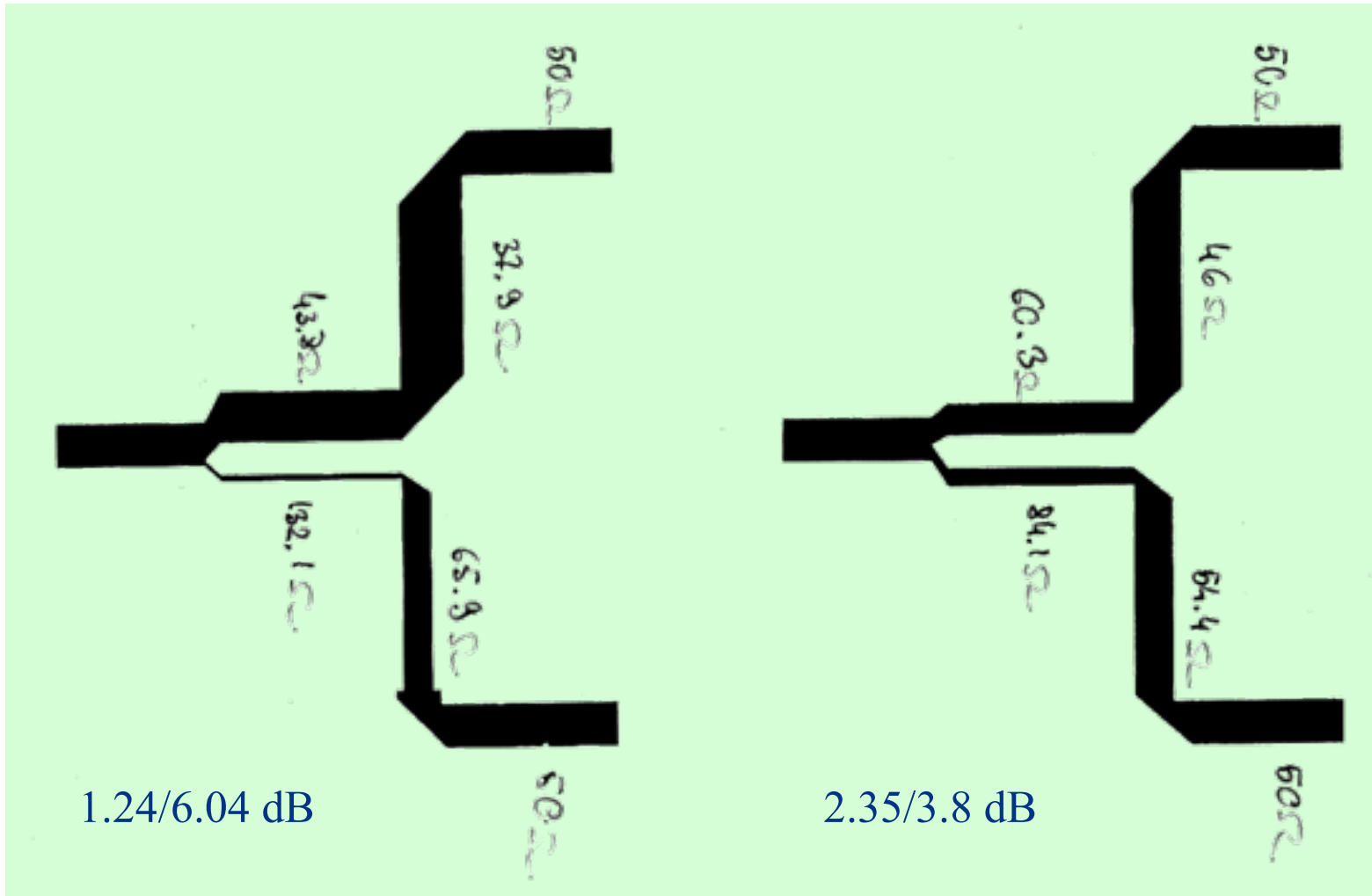Typical examples of Wilkinson power dividers with unequal power split



Summary of lecture 8

- Read chapter 7.1-7.4 (dividers).
 - Attenuators, phase shifters
 - Directional couplers

Further reading

- Ernest J. Wilkinson, “An N-Way Hybrid Power Divider,” IRE Transactions on Microwave Theory and Techniques, vol. 8, no. 1, pp. 116–118, 1960.
- S. Cohn and R. Levy, “History of Microwave Passive Components with Particular Attention to Directional Couplers,” IEEE Transactions on Microwave Theory and Techniques, vol. 32, no. 9, pp. 1046–1054, 1984.