

MCC120

Microwave Electronics, Chalmers University of Technology, MC2, building B, 6th floor.

Exam in **FOUNDATIONS FOR MICROWAVE ENGINEERING** for MPMPE and E4/F4

Tuesday, December 14, 2010, 8:30-12:30, M building

Teacher: Docent Piotr Starski
Questions: Docent Piotr Starski

tel.: 031-772 17 34
tel.: 031-772 17 34

Solutions are in my office.

The inspection of the results can be done in my office on Tuesday, January 4, 2011, 10:30-11:30.

The final results will be sent to registrar office on Monday, January 10, 2011.

The limits for the grades are as follows:


- *7.5 credits* → *grade 3*
- *11 credits* → *grade 4*
- *14.5 credits* → *grade 5*

The following items are allowed on the examination:

- *Any type of calculator*
- *Copies of the lectures viewgraphs*
- *"Foundations for microwave engineering" by Collin*
- *A conversion table distributed in the tutorials*
- *Mathematical tables*

It is imperative to clearly explain how the results have been obtained

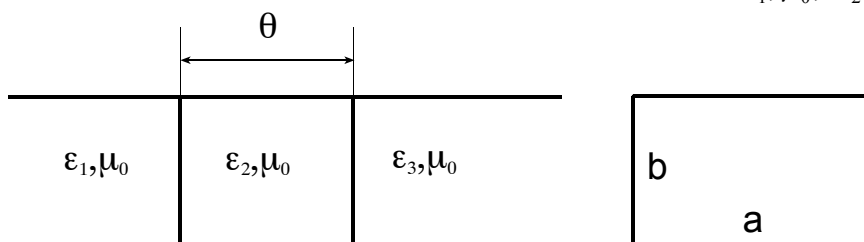-
1. A rectangular waveguide is filled with three different dielectrics: ϵ_1, μ_0 , ϵ_2, μ_0 and ϵ_3, μ_0




We know also, that $\epsilon_1 < \epsilon_2 < \epsilon_3$. Calculate the length of the section in the middle, θ , and ϵ_2 , to obtain maximal power transfer at center frequency from the left to the right.

Assume that the waveguide is working in the dominant mode and $a=2b$.

2. We have an air filled circular waveguide. The waveguide is excited in *TM* modes. Calculate the frequency f as a function of cut-off frequency f_c to obtain the lowest possible attenuation (consider only metallic losses).


3. For an ideal transformer

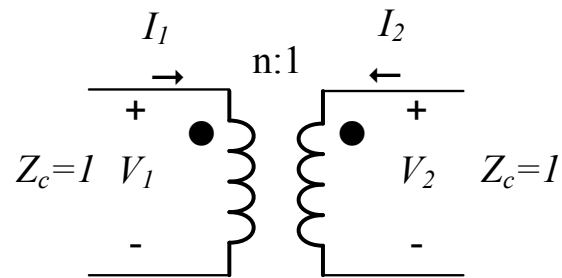

derive the s matrix starting from the given currents and voltages.


4. Consider a 3 port network which is lossless and reciprocal. We know that $s_{13}=s_{23}$ and $s_{11}=s_{22}$. Port 2 of the network is loaded with a matched load. Show that by loading port 3 with an appropriate reactance port 1 can be matched.

5. Analyze the circuit below:

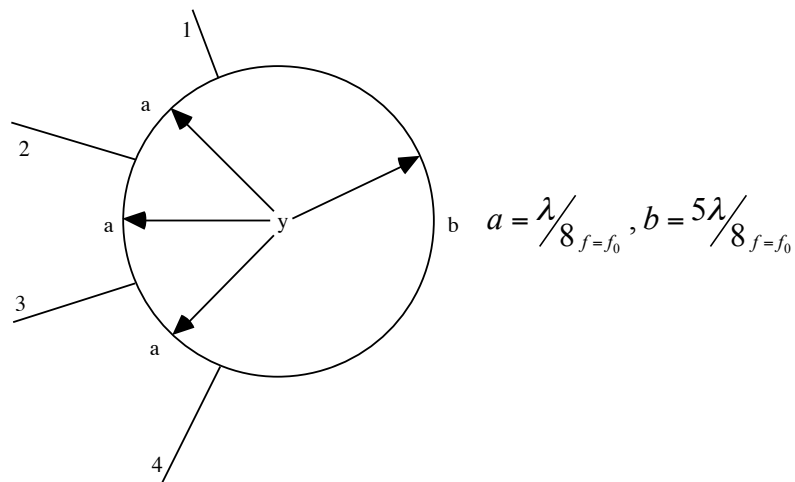

The ring has normalized admittance y . Calculate s parameters if the ring is fed in port 1. Calculate y to obtain around 3 dB power split (exact equal power split is not possible).

6. Consider the circuit below:

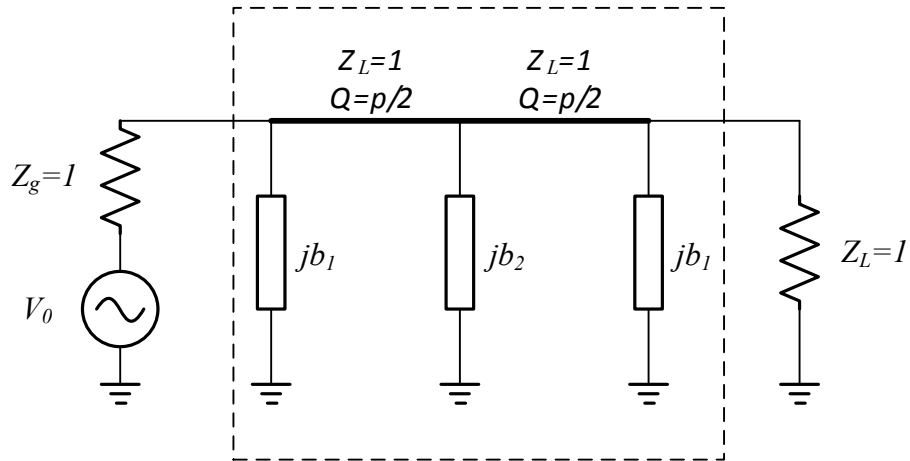

Calculate b_2 as the function of b_1 if the circuit in the dashed lines is matched. What is the transmission phase of this circuit expressed in b_1 ? Is it possible to have different components at match, i.e. inductor or capacitor at the same time as b_1 and b_2 ?